

Question 1. Branching

1.0 For the killed end (Dirichlet) boundary condition, we have

$$R_{in} = R_{\infty} \tanh(L)$$

where R_{∞} is the input resistance for a semi-infinite cable given by

$$R_{\infty} = \sqrt{\frac{4\tilde{r}_m\tilde{r}_a}{\pi^2 d^3}}$$

and L is the electrotonic length given by

$$L = \frac{l}{\lambda}$$

where λ is the length constant defined as

$$\lambda = \sqrt{\frac{4\tilde{r}_m d}{4\tilde{r}_a}}$$

\tilde{r}_m and \tilde{r}_a are the specific membrane and axial resistances, respectively. Hence, for the input resistance for compartment 2 we have

$$R_{in,2} = \sqrt{\frac{4 \cdot 1 \cdot 1}{\pi^2 (5 \cdot 10^{-6})^3}} \cdot \tanh(0.089) = 5.05 \text{ M}\Omega$$

For the sealed end (Neumann) we have

$$R_{in} = R_{\infty} \coth(L)$$

Accordingly, for compartment 3 we have

$$R_{in,3} = \sqrt{\frac{4 \cdot 1 \cdot 1}{\pi^2 (4 \cdot 10^{-6})^3}} \cdot \coth(0.1) = 798.45 \text{ M}\Omega$$

Note the following relationship

$$R_{L,1}^{-1} = (R_{in,2}^{-1} + R_{in,3}^{-1})$$

Therefore, the leak resistance for compartment 1 is

$$R_{L,1} = \left((5.05 \cdot 10^6)^{-1} + (798.45 \cdot 10^6)^{-1} \right)^{-1} = 5.02 \text{ }\mu\Omega$$

1.1 To compute the potential $V(\infty)$ in response to a constant current $I_0 = 1 \text{ nA}$ we need to assume that the system has relaxed to a stationary solution and apply the formula for a finite cable potential as shown below

$$V(X) = E_m + R_{\infty} I_0 \frac{R_L \cosh(L - X) + R_{\infty} \sinh(L - X)}{R_L \sinh(L) + R_{\infty} \cosh(L)}$$

where R_∞ for compartment 1 is computed as shown above and X is defined as

$$X = \frac{x}{\lambda}$$

where x is the distance along the compartment. Thus, plugging in the numbers and setting $t = \infty$ and $x = 0$ gives

$$X(\infty) = 6.388 \text{ mV}$$

From this we can compute the input resistance $R_{in,1}$

$$R_{in,1} = \frac{6.338 \cdot 10^{-3}}{10^{-9}} = 6.388 \text{ M } \Omega$$

1.2 To get the current entering compartments 2 & 3, I_L , we compute

$$V(X = L) = E_m + R_\infty I_0 \frac{R_L \cosh(0) + R_\infty \sinh(0)}{R_L \sinh(L) + R_\infty \cosh(L)} = 4.993 \cdot 10^{-15} \text{ A}$$

And the corresponding I_L is then

$$I_L = \frac{V(L)}{R_L} = 0.995 \text{ nA}$$

Then we apply the current divider formula for resistors connected in parallel

$$I_X = \frac{R_T}{R_X + R_T} I_T$$

Where I_X is the current through the resistor with resistance R_X , and I_T and R_T are the total current entering and the total resistance in parallel, respectively. Thus, by substituting the values we get

$$I_2 = 9.883 \text{ nA}, \text{ and } I_3 = 0.0625 \text{ nA}$$

1.3 Assuming that compartment 2 is terminated by a sealed end will change its input resistance and, consequently, the leak resistance for compartment 1. The new input resistance for compartment 2 is thus

$$R_{in,2} = \sqrt{\frac{4 \cdot 1 \cdot 1}{\pi^2 (5 \cdot 10^{-6})^3}} \cdot \coth(0.089) = 641.46 \text{ M}\Omega$$

Hence, $R_{L,1}$ becomes

$$R_{L,1} = \left((641.46 \cdot 10^6)^{-1} + (798.45 \cdot 10^6)^{-1} \right)^{-1} = 355.70 \text{ M}\Omega$$

And by applying the above formula for $V(\infty)$ we get

$$V(\infty) = 104 \text{ mV}$$

Question 2. Equivalent Cylinder

- 2.1 No, this branching model cannot be simplified by an equivalent cylinder model, for the branching compartments do not follow the ' $\frac{3}{2}$ diameter rule', which must satisfy

$$(d_1)^{\frac{3}{2}} = (d_2)^{\frac{3}{2}} + (d_3)^{\frac{3}{2}}$$

where d_1 , d_2 , and d_3 are the corresponding compartment diameters.

- 2.2 To find the required diameters, we can use the formula for electrotonic lengths which must hold if we are to simplify this two-branch model. The formula appears below

$$L_i = \frac{l_i}{\lambda_i} = \frac{l_j}{\lambda_j} = L_j \quad \text{for } i, j > 1$$

Hence, using our definition above and plugging in the numbers gives us

$$\frac{260 \cdot 10^{-6}}{\frac{\sqrt{d_1}}{2}} = \frac{100 \cdot 10^{-6}}{\frac{\sqrt{d_3}}{2}} = 0.14 \mu\text{m}$$

$$d_1 = 13.8 \mu\text{m}, \text{ and } d_3 = 2.04 \mu\text{m}$$